

Understanding Operational Amplifiers

Cheng Zhang

Nan Xia

Alexander Gollin

Kenneth Young

Patrick Powers



Outline

- Cheng - History
- Pat - OP AMP Construction/design
- Alex - OP Amp Application Circuits
- Ken - Effect of Input offset voltage
- Nan - Effect of Slew Rate, Packaging, Conclusion



History

1941	First vacuum tube op-amp	Karl D. Swartzel Jr.
1947	First op-amp with non-inverting input	John R. Ragazzini
1949	First chopper-stabilized op-amp	Edwin A. Goldberg
1961	Discrete IC op-amp	



History Continued

1963	First monolithic IC op-amp	Bob Widlar
1970	First high-speed, low-input current FET design	
1972	Single sided supply op-amps being produced	




Op Amp Construction

- Integrated Circuit(IC) Main Categories:
 - Linear ICs
 - Performs amplification or linear operations on signals.
 - Monolithic ("one stone") Circuits
 - The entire circuit is embedded upon a single piece of semiconductor.



μA741 Op-Amp

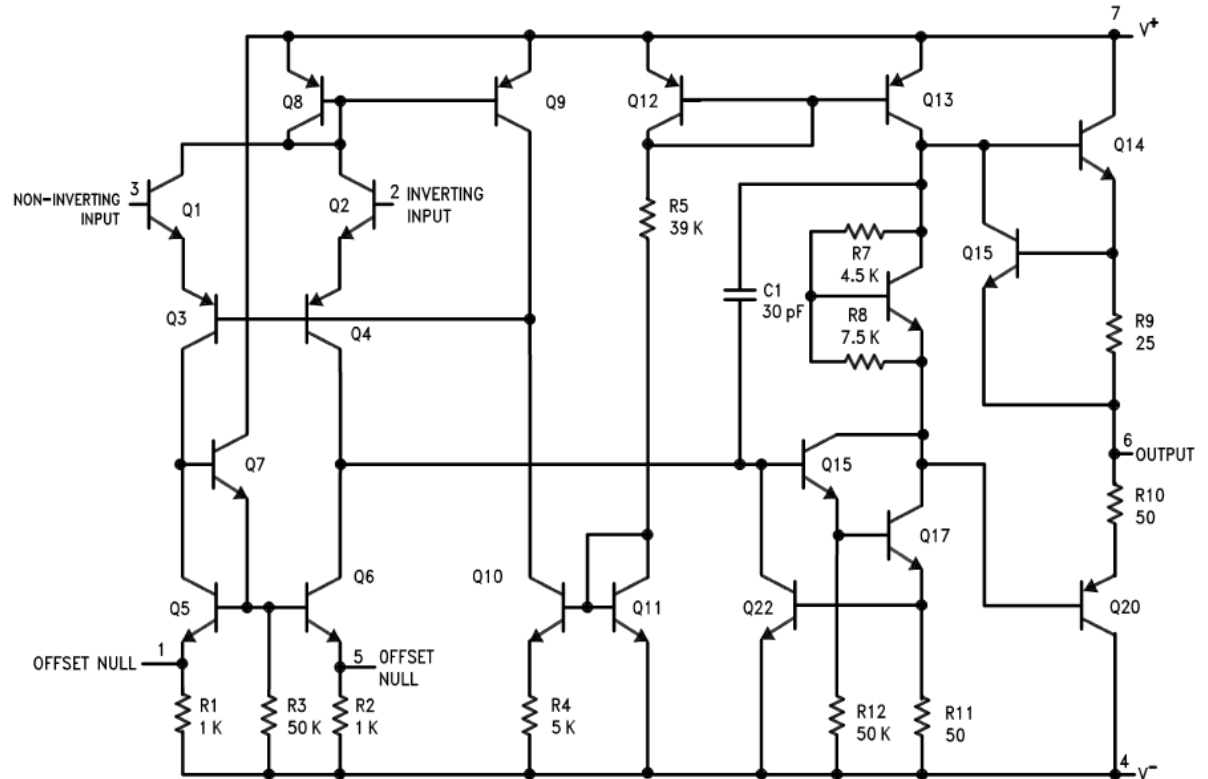- Bias Circuit
- Input Stage
- Intermediate Stage
- Output Stage
- Short-circuit Protection





Internal Schematic from LM741 Datasheet


00934101




Monolithic Building Blocks

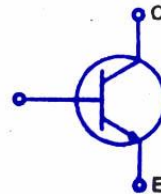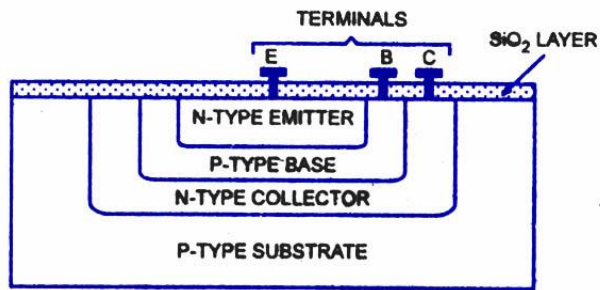



Transistor

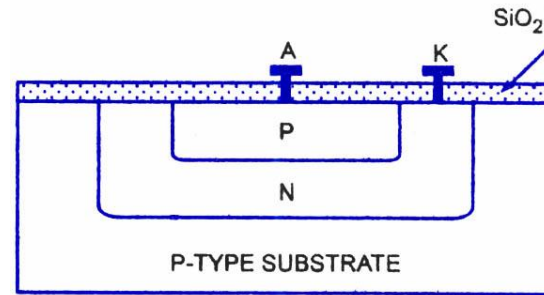

Diode

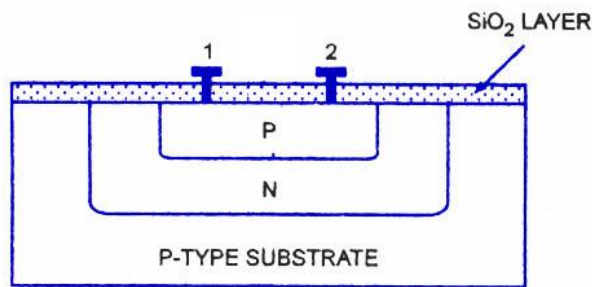


IC Diffused Resistor

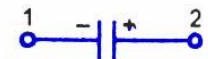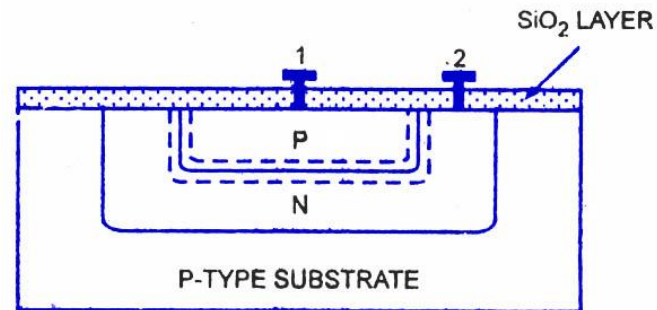


IC Diffused Capacitor



Biassing Circuit

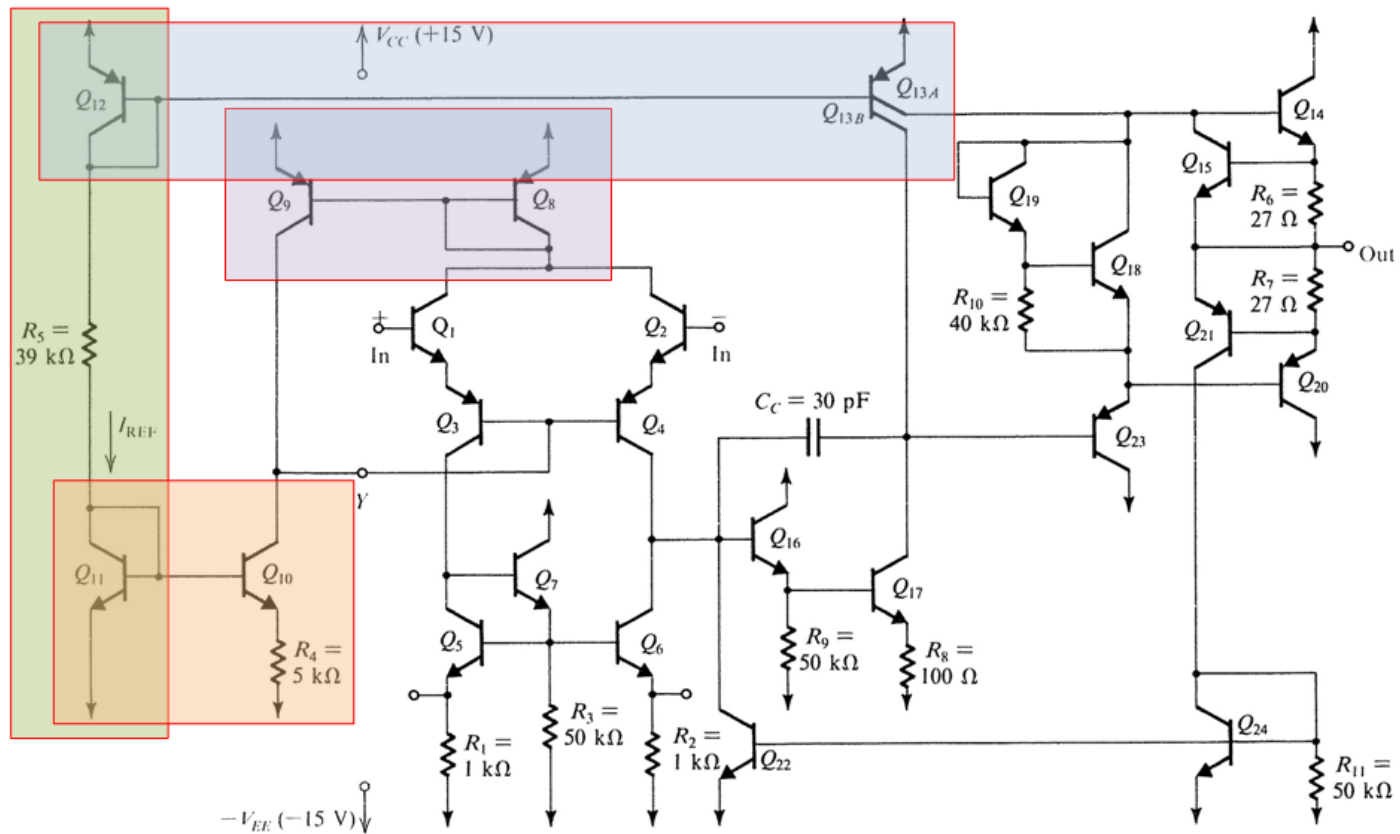

Biassing Circuit

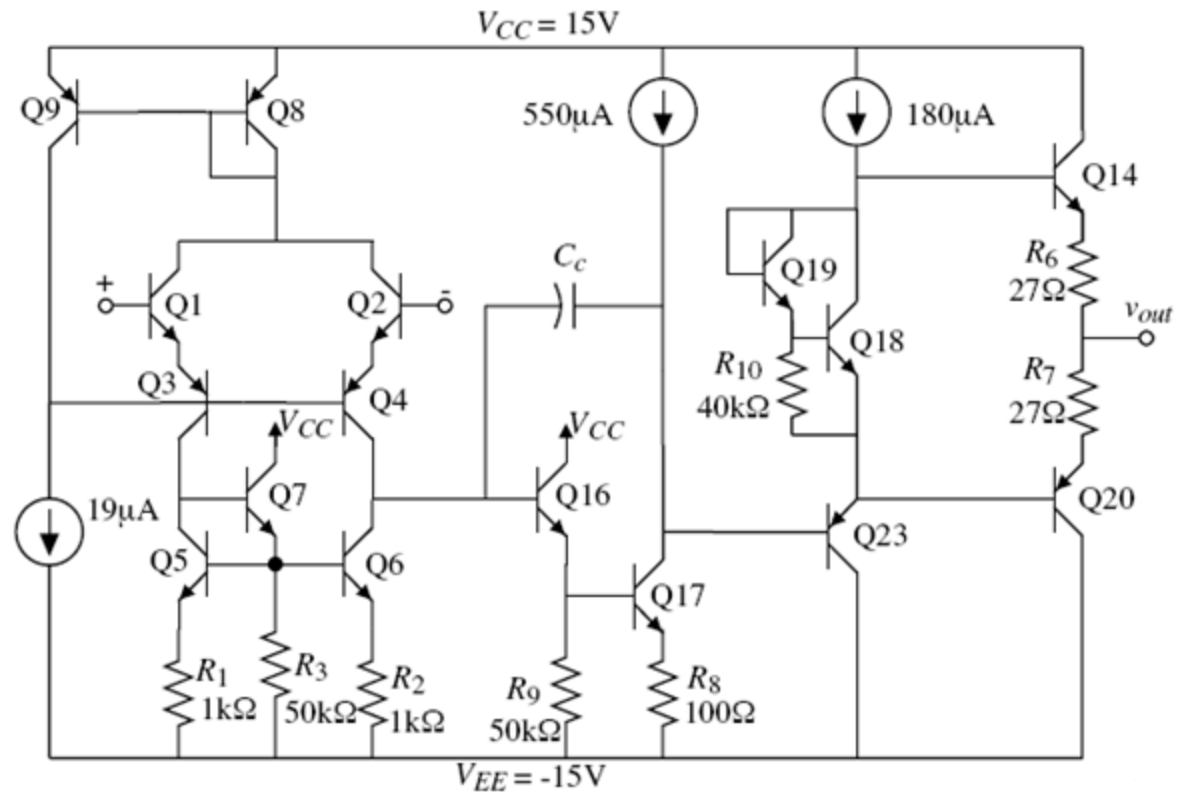

$$I_{ref} = \frac{V_{CC} - V_{EE} - 2V_{BE}}{R_5} = 733\mu A$$

$$I_{13B} = 0.75 I_{ref} = 550\mu A$$

$$I_{13A} = 0.25 I_{ref} = 180\mu A$$

$$I_{10} = \frac{V_t}{R_4} [\ln(I_{ref}) - \ln(I_{10})] = 19\mu A$$




Input Stage

- Q1, Q2 are emitter followers.
- Q3, Q4 in common-base configuration serve as differential amplifier, level shifters and protect Q1, Q2 against emitter-base junction breakdown.
- Q5, Q6, Q7 and R1, R2, R3 provide the load (active load) for the differential amplifier.



Intermediate Stage

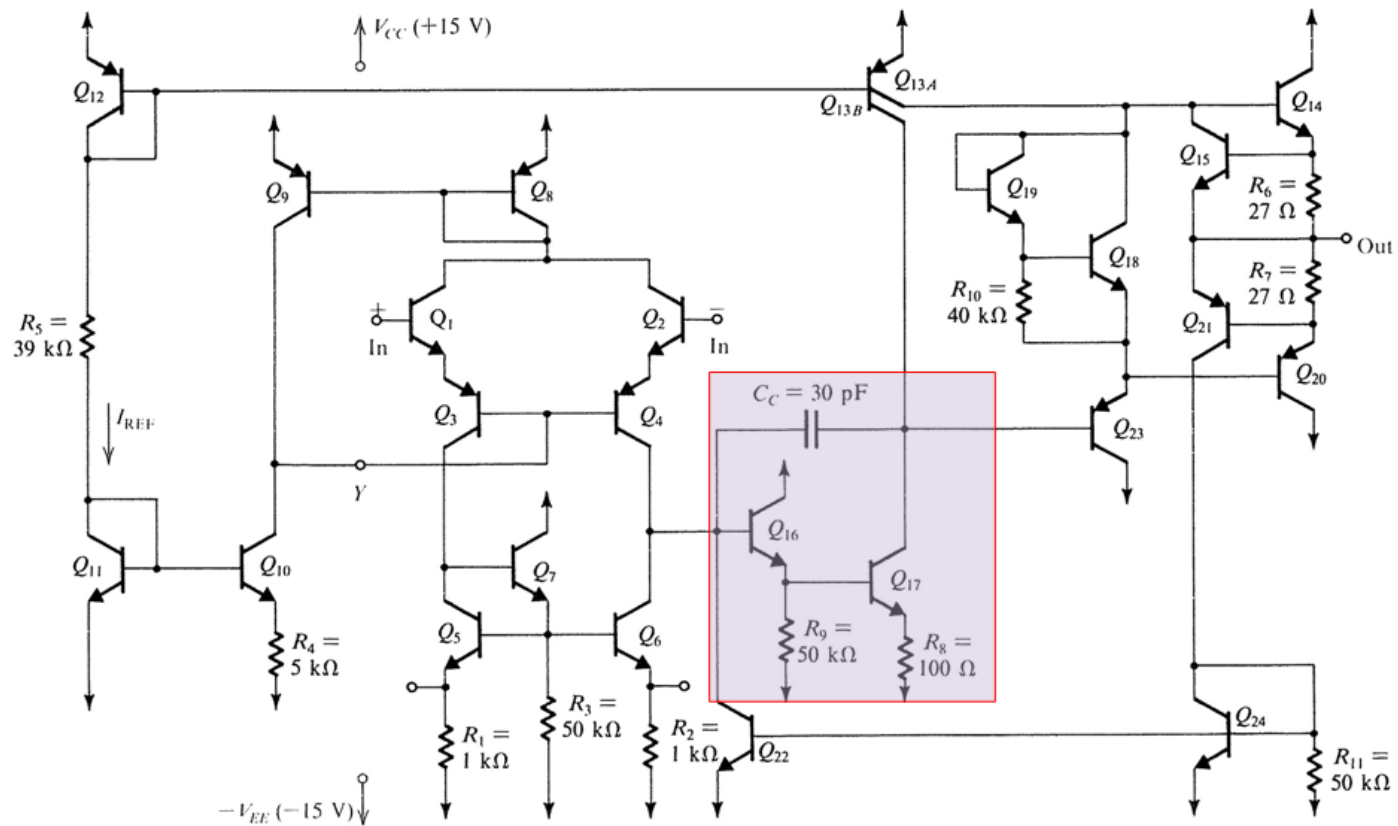


Intermediate Stage

- Q16 is an emitter follower.
- Q17 is a common-emitter amplifier, loaded by Q13B.
 - $GAIN \approx (g_{m-Q17})(r_{o-Q13B})$
- Cc is the internal compensation cap used to maintain stability when the op-amp is used in a feedback configuration.



Output Stage

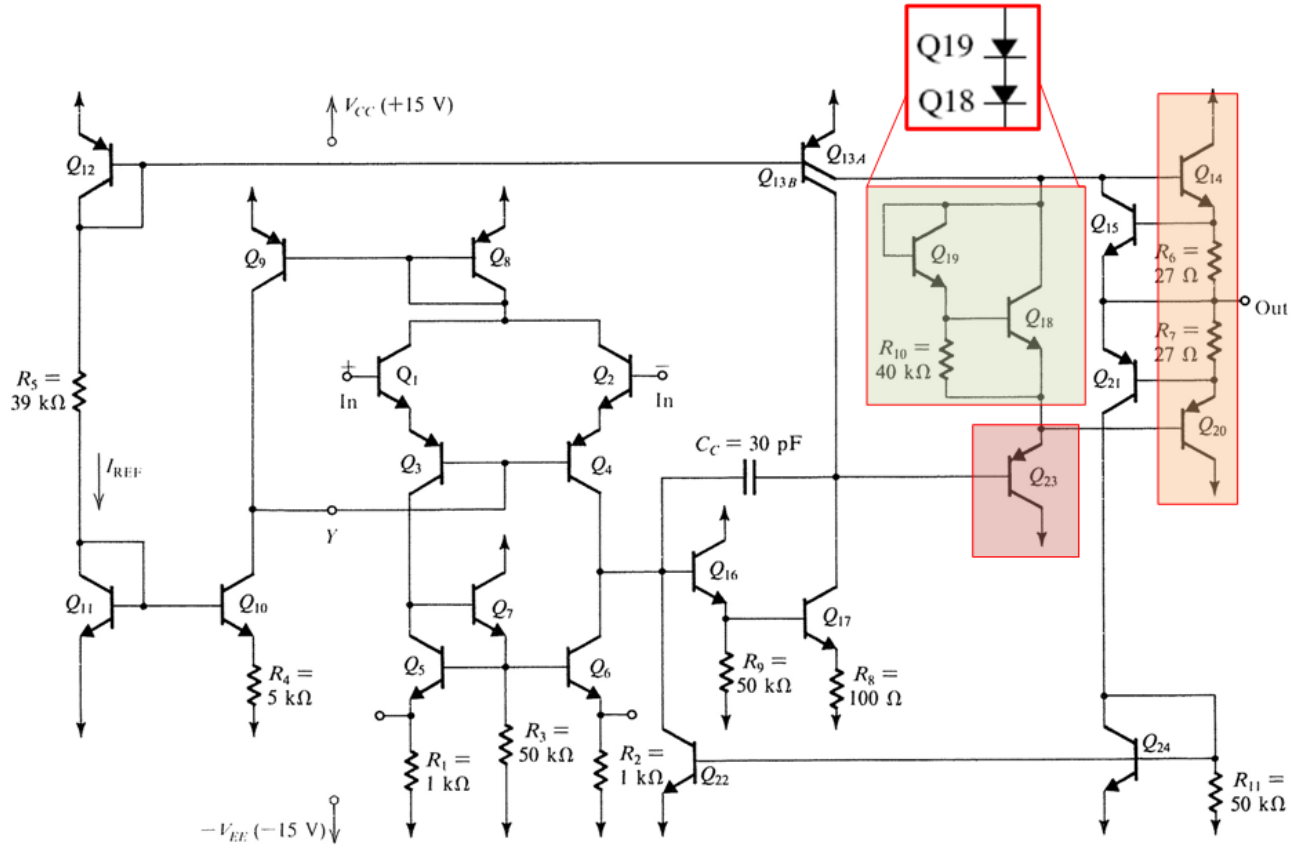


Output Stage

- Q23 is an emitter follower.
- Q14, Q20 are a complementary push-pull, or Class AB amplifier.
- Q19, Q18 are a Darlington-pair, but act similar to diodes. They maintain a V_{BE} drop to smooth out the crossover distortion of Q14, Q20.



Short-circuit Protection

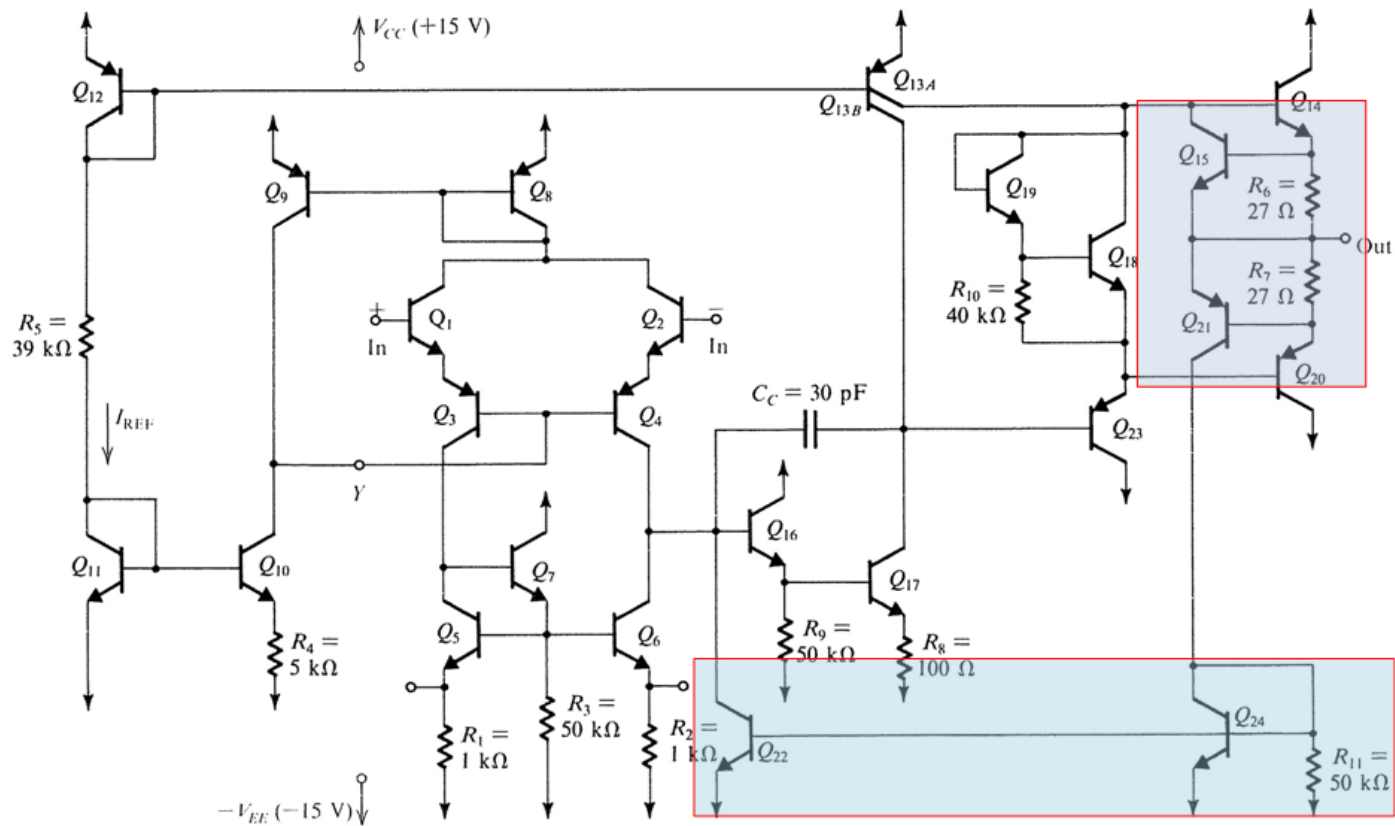


Short-circuit Protection

- Q15, Q21 are normally off.
- If too much current is being output ($\sim 25\text{mA}$), the voltage drop across R6, R7 will turn Q15, Q21 on to bleed off the current via Q22, Q24 current mirror.




Op-amp Design Applications

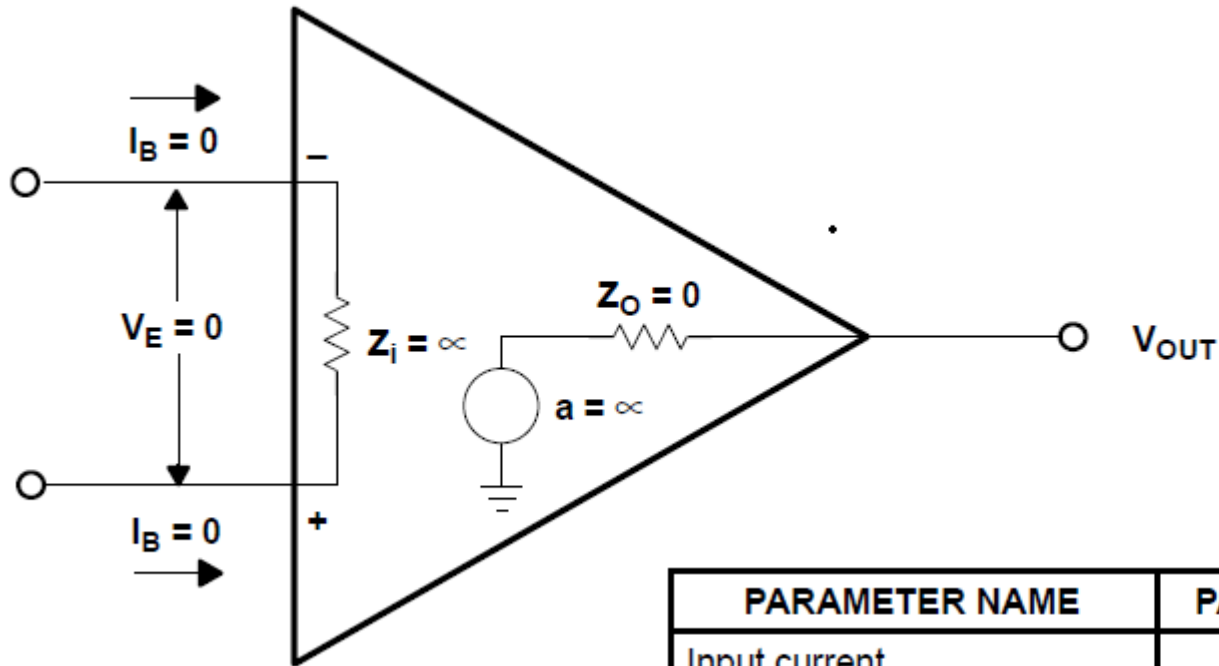


PARAMETER NAME	PARAMETERS SYMBOL	VALUE
Input current	I_{IN}	0
Input offset voltage	V_{OS}	0
Input impedance	Z_{IN}	∞
Output impedance	Z_{OUT}	0
Gain	a	∞



Simple Buffer Circuit or Voltage Follower

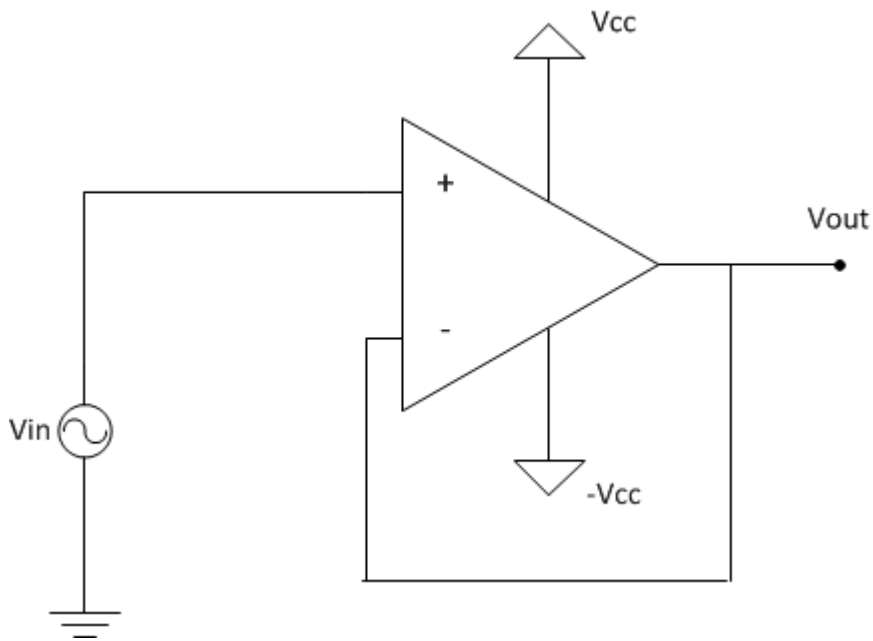


Typical 8-pin Op-Amp Layout

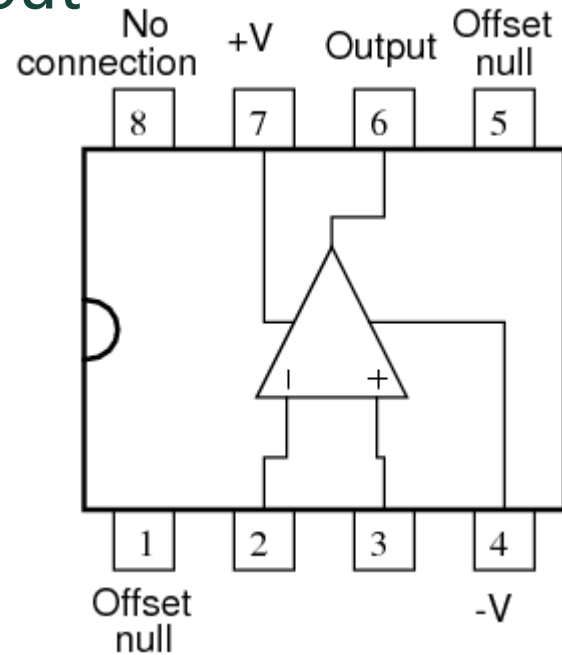


Amplifier Circuits

Non-Inverting

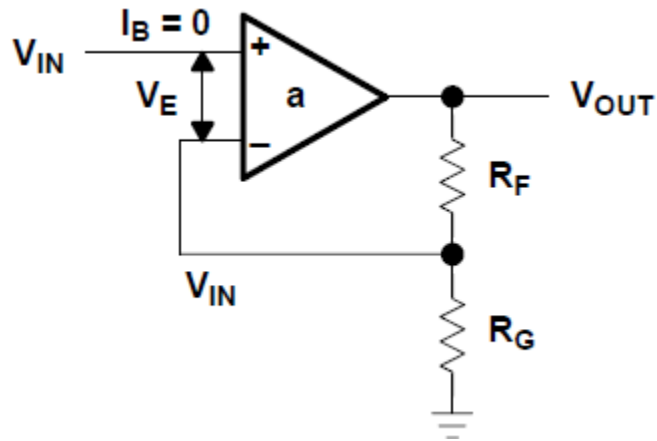

$$\frac{V_{OUT}}{V_{IN}} = \frac{R_G + R_F}{R_G} = 1 + \frac{R_F}{R_G}$$


Inverting

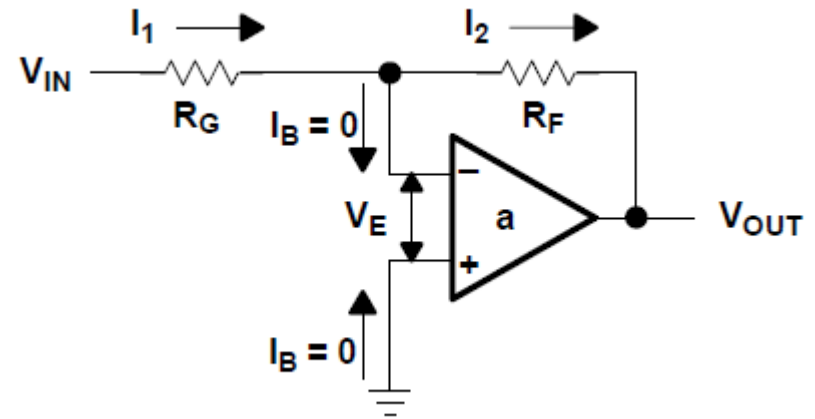

$$\frac{V_{OUT}}{V_{IN}} = -\frac{R_F}{R_G}$$




Adder

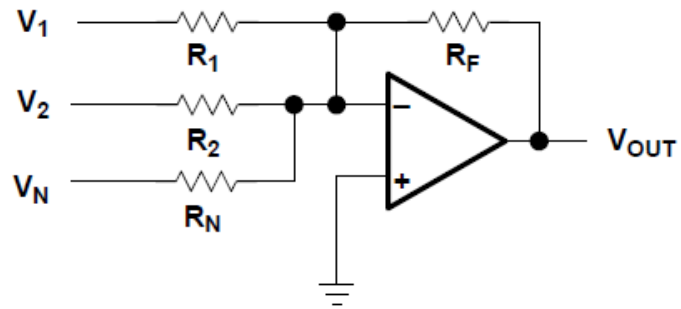

$$V_{OUT} = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_N} V_N \right)$$


Differential

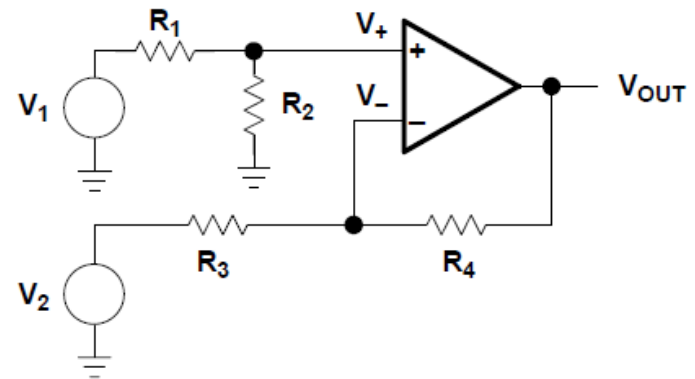

$$V_{OUT} = (V_1 - V_2) \frac{R_4}{R_3}$$





Non-Inverting Summing Amplifier

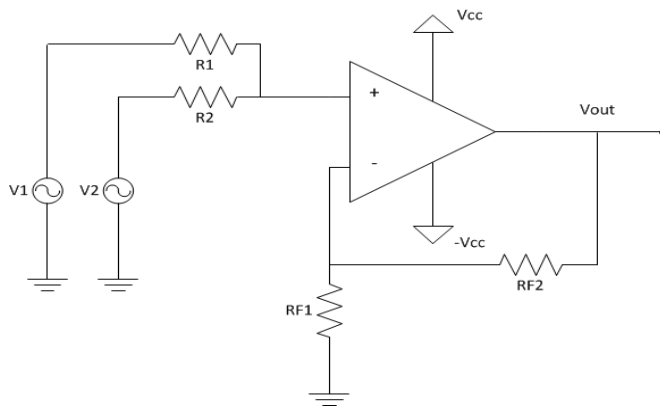


$$V_{out} = \left(1 + \frac{R_{f2}}{R_{f1}}\right) \cdot \left(V_1 \cdot \frac{R_2}{R_1 + R_2} + V_2 \cdot \frac{R_1}{R_1 + R_2}\right)$$




Integrator

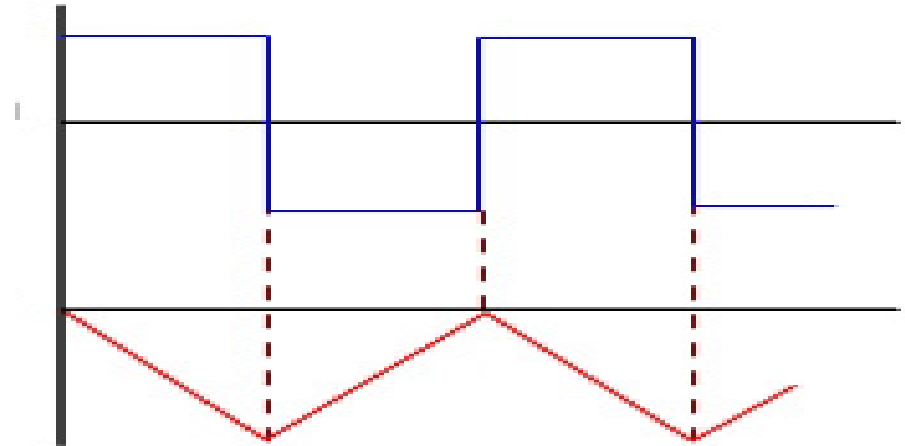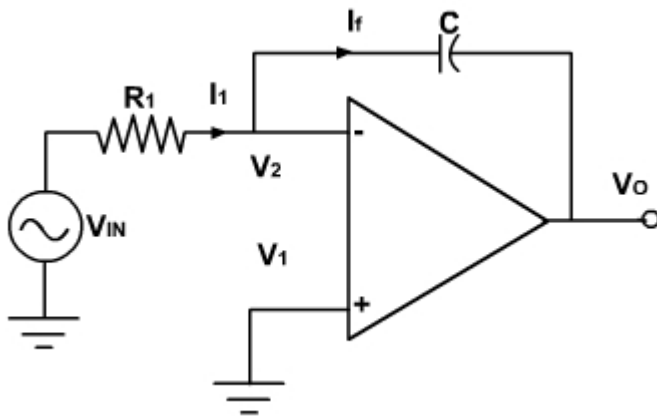

Active Filter Design

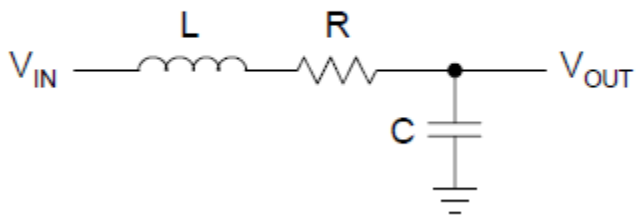

Passive

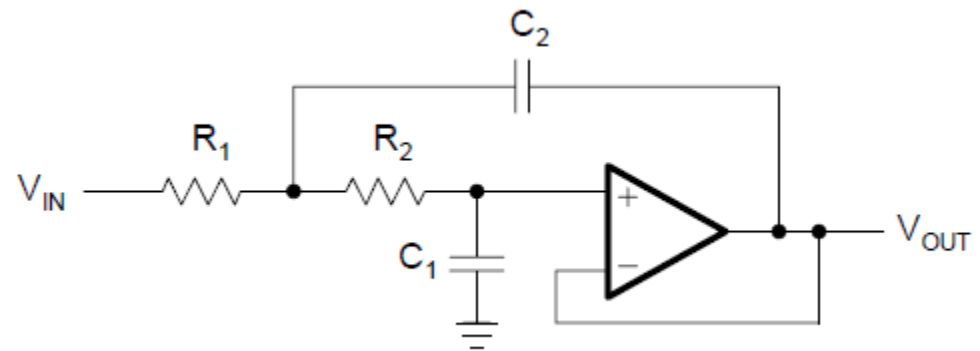

Active



OP AMP Specifications

Some Specifications to be aware of when using Operational Amplifiers in your circuits.

- Input Offset Voltage- Input Offset Null Pins
- Slew Rate



LM741 Datasheet


Electrical Characteristics (Note 5)											
Parameter	Conditions	LM741A			LM741			LM741C			Units
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Input Offset Voltage	$T_A = 25^\circ\text{C}$ $R_S \leq 10\text{ k}\Omega$ $R_S \leq 50\Omega$		0.8	3.0		1.0	5.0		2.0	6.0	mV mV
	$T_{AMIN} \leq T_A \leq T_{AMAX}$ $R_S \leq 50\Omega$ $R_S \leq 10\text{ k}\Omega$			4.0			6.0			7.5	mV mV
Average Input Offset Voltage Drift				15							$\mu\text{V}/^\circ\text{C}$
Input Offset Voltage Adjustment Range	$T_A = 25^\circ\text{C}, V_S = \pm 20\text{V}$	± 10				± 15			± 15		mV
Input Offset Current	$T_A = 25^\circ\text{C}$		3.0	30		20	200		20	200	nA
	$T_{AMIN} \leq T_A \leq T_{AMAX}$			70		85	500			300	nA
Average Input Offset Current Drift				0.5							$\text{nA}/^\circ\text{C}$
Input Bias Current	$T_A = 25^\circ\text{C}$		30	80		80	500		80	500	nA
	$T_{AMIN} \leq T_A \leq T_{AMAX}$			0.210			1.5			0.8	μA
Input Resistance	$T_A = 25^\circ\text{C}, V_S = \pm 20\text{V}$	1.0	6.0		0.3	2.0		0.3	2.0		$\text{M}\Omega$
	$T_{AMIN} \leq T_A \leq T_{AMAX},$ $V_S = \pm 20\text{V}$	0.5									$\text{M}\Omega$
Input Voltage Range	$T_A = 25^\circ\text{C}$							± 12	± 13		V
	$T_{AMIN} \leq T_A \leq T_{AMAX}$				± 12	± 13					V



Electrical Characteristics (Note 5) (Continued)


Parameter	Conditions	LM741A			LM741			LM741C			Units
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Large Signal Voltage Gain	$T_A = 25^\circ\text{C}$, $R_L \geq 2\text{ k}\Omega$ $V_S = \pm 20\text{V}$, $V_O = \pm 15\text{V}$ $V_S = \pm 15\text{V}$, $V_O = \pm 10\text{V}$	50									V/mV V/mV
	$T_{AMIN} \leq T_A \leq T_{AMAX}$, $R_L \geq 2\text{ k}\Omega$, $V_S = \pm 20\text{V}$, $V_O = \pm 15\text{V}$ $V_S = \pm 15\text{V}$, $V_O = \pm 10\text{V}$	32									V/mV V/mV
	$V_S = \pm 5\text{V}$, $V_O = \pm 2\text{V}$	10			25			15			V/mV
Output Voltage Swing	$V_S = \pm 20\text{V}$ $R_L \geq 10\text{ k}\Omega$ $R_L \geq 2\text{ k}\Omega$	± 16 ± 15									V V
	$V_S = \pm 15\text{V}$ $R_L \geq 10\text{ k}\Omega$ $R_L \geq 2\text{ k}\Omega$				± 12 ± 10	± 14 ± 13		± 12 ± 10	± 14 ± 13		V V
Output Short Circuit Current	$T_A = 25^\circ\text{C}$	10	25	35		25			25		mA
	$T_{AMIN} \leq T_A \leq T_{AMAX}$	10		40							mA
Common-Mode Rejection Ratio	$T_{AMIN} \leq T_A \leq T_{AMAX}$ $R_S \leq 10\text{ k}\Omega$, $V_{CM} = \pm 12\text{V}$ $R_S \leq 50\Omega$, $V_{CM} = \pm 12\text{V}$	80	95		70	90		70	90		dB dB
Supply Voltage Rejection Ratio	$T_{AMIN} \leq T_A \leq T_{AMAX}$, $V_S = \pm 20\text{V}$ to $V_S = \pm 5\text{V}$ $R_S \leq 50\Omega$ $R_S \leq 10\text{ k}\Omega$	86	96								dB dB
					77	96		77	96		
Transient Response Rise Time Overshoot	$T_A = 25^\circ\text{C}$, Unity Gain		0.25	0.8		0.3			0.3		μs %
			6.0	20		5			5		
Bandwidth (Note 6)	$T_A = 25^\circ\text{C}$	0.437	1.5								MHz
Slew Rate	$T_A = 25^\circ\text{C}$, Unity Gain	0.3	0.7			0.5			0.5		V/ μs
Supply Current	$T_A = 25^\circ\text{C}$					1.7	2.8		1.7	2.8	mA

What is Input Offset Voltage?

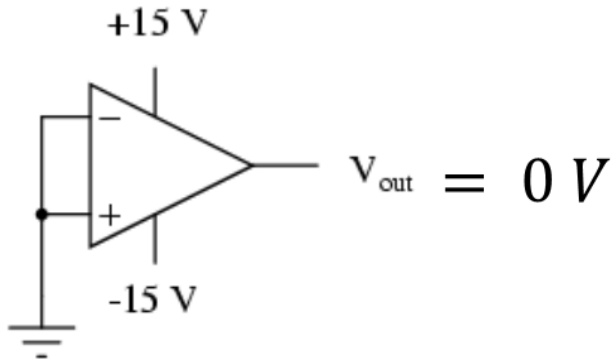

Ideal OP AMP

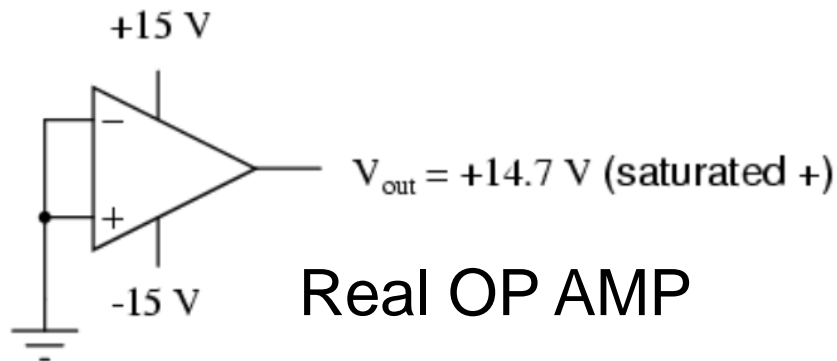In an Ideal Op Amp the output should be exactly 0v with inputs shorted.





Real OP AMP

However In a real OP Amp there will be some output voltage when the inputs are shorted due to slight differences in the internal OP Amp transistors



What Causes Input Offset Voltage?

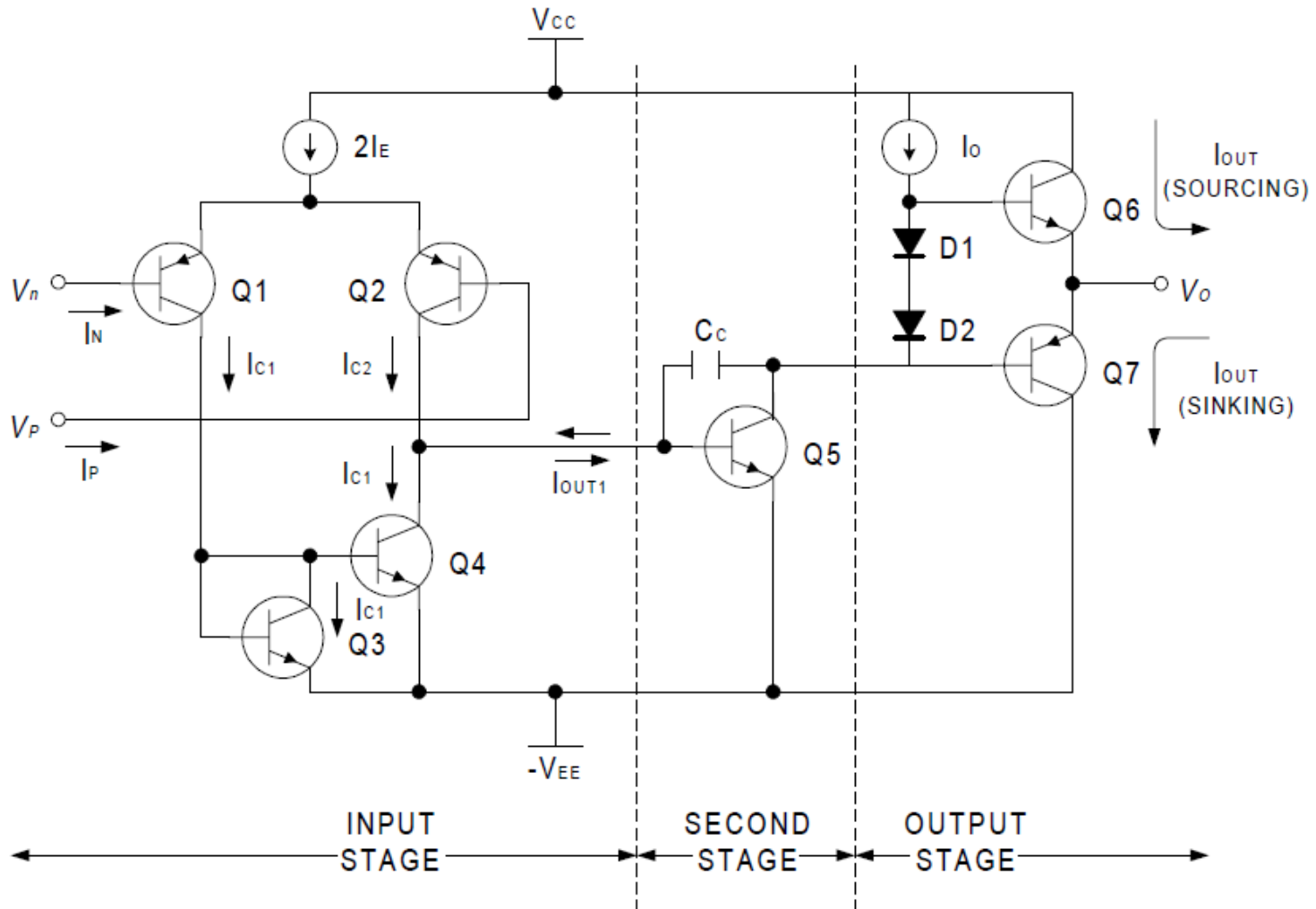

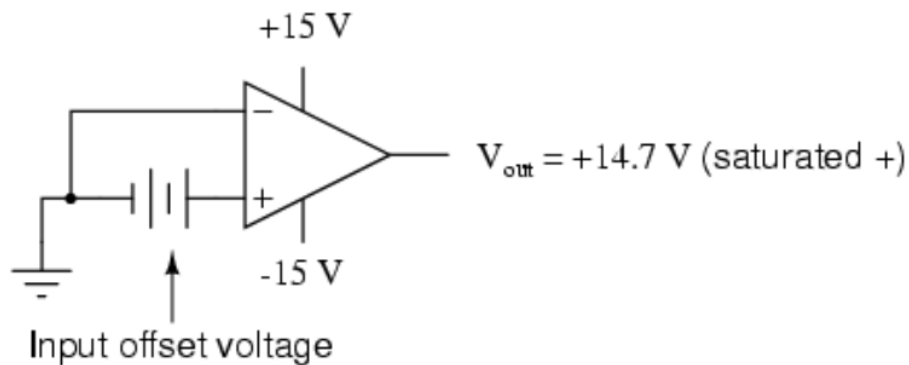


Typically 0 to 10 mV

The Input Offset Voltage can be modeled as a small voltage always present at one of the inputs to an Ideal Op Amp.



Effect of Input Offset Voltage

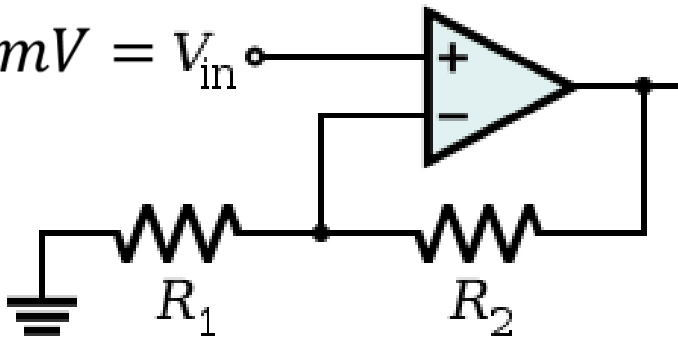


$50 \text{ mV} = V_{in}$

$$V_{out} = V_{in} * \left(1 + \frac{R_2}{R_1} \right)$$

$$= 50 \text{ mV} * (1 + 99)$$

$$= 5 \text{ V}$$

$R_1 = 1 \text{ K}$ $R_2 = 99 \text{ K}$

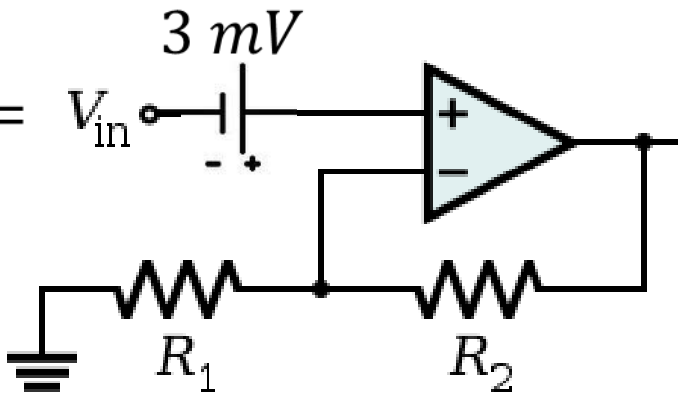

$50 \text{ mV} = V_{in}$

3 mV

$$V_{out} = (V_{in} + 3 \text{ mV}) * \left(1 + \frac{R_2}{R_1} \right)$$

$$= 53 \text{ mV} * (1 + 99)$$



$$= 5.3 \text{ V OR } 4.7 \text{ V}$$

$R_1 = 1 \text{ K}$ $R_2 = 99 \text{ K}$


LM741 Null Pins


Some Op Amps have NULL Pins which allow adjustment to compensate for Input Offset Voltage.

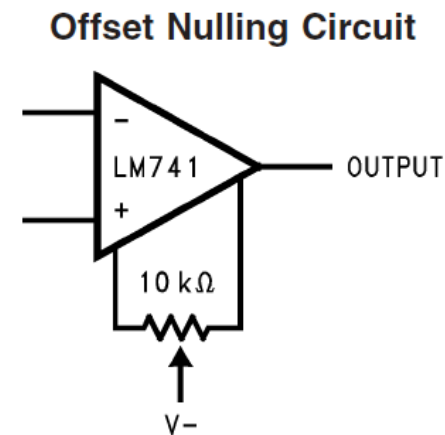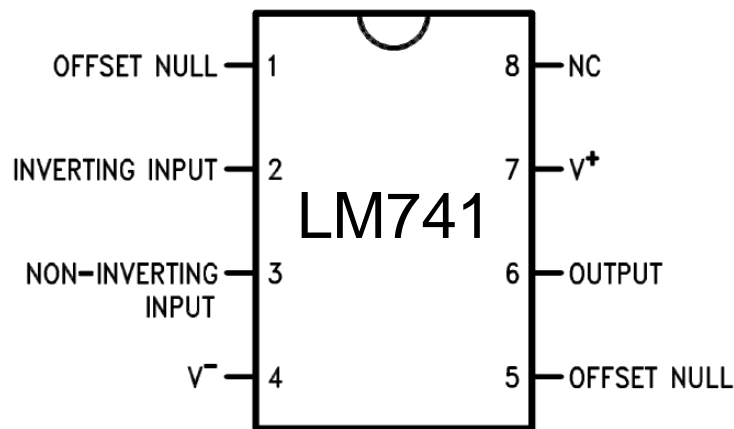- LM741 Has Null Pins
- LM324 Does NOT have Null Pins




LM741 Schematic

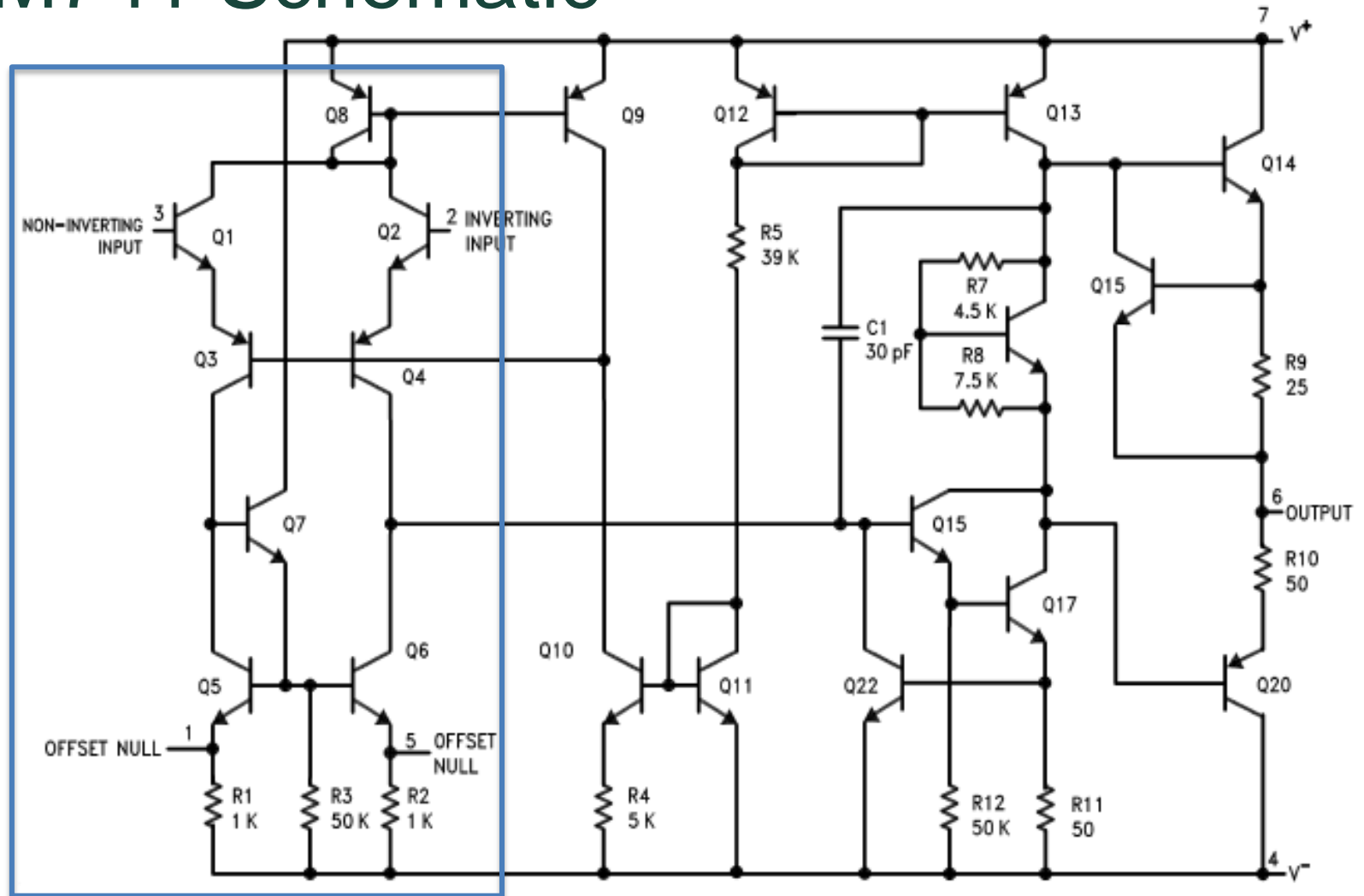

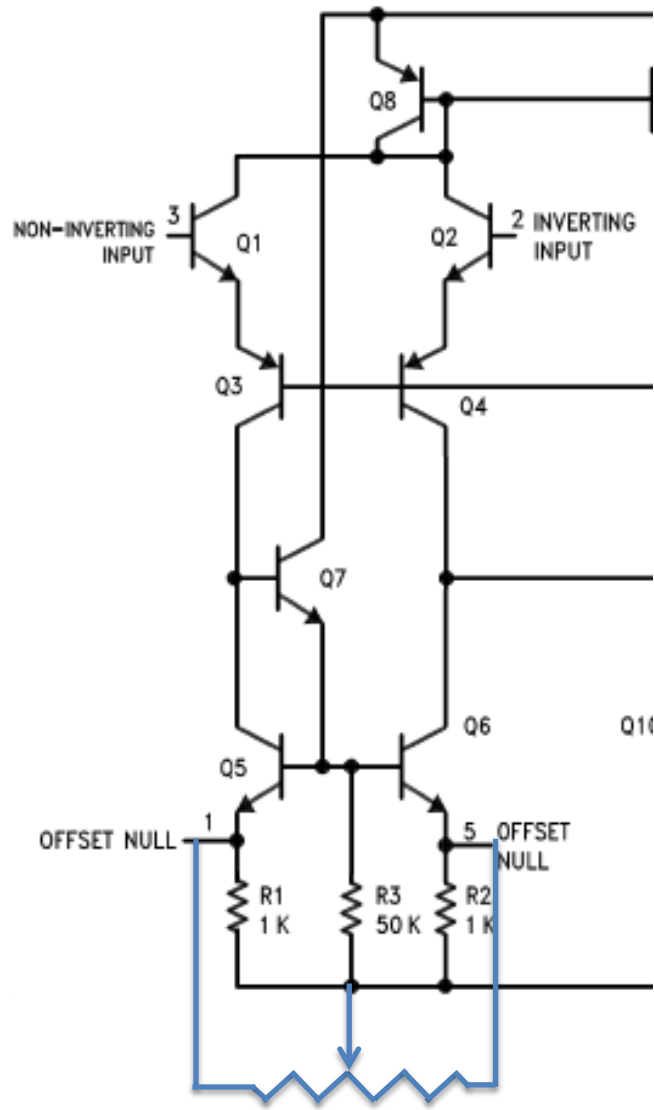

LM741 Input


Offset Nulling Circuit

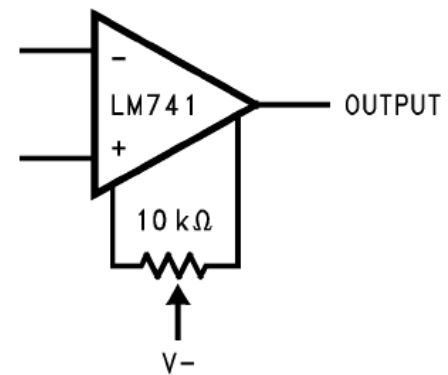

Slew Rate

The Slew Rate of an Op Amp is the maximum rate of change in the output voltage expressed in volts/ μ s

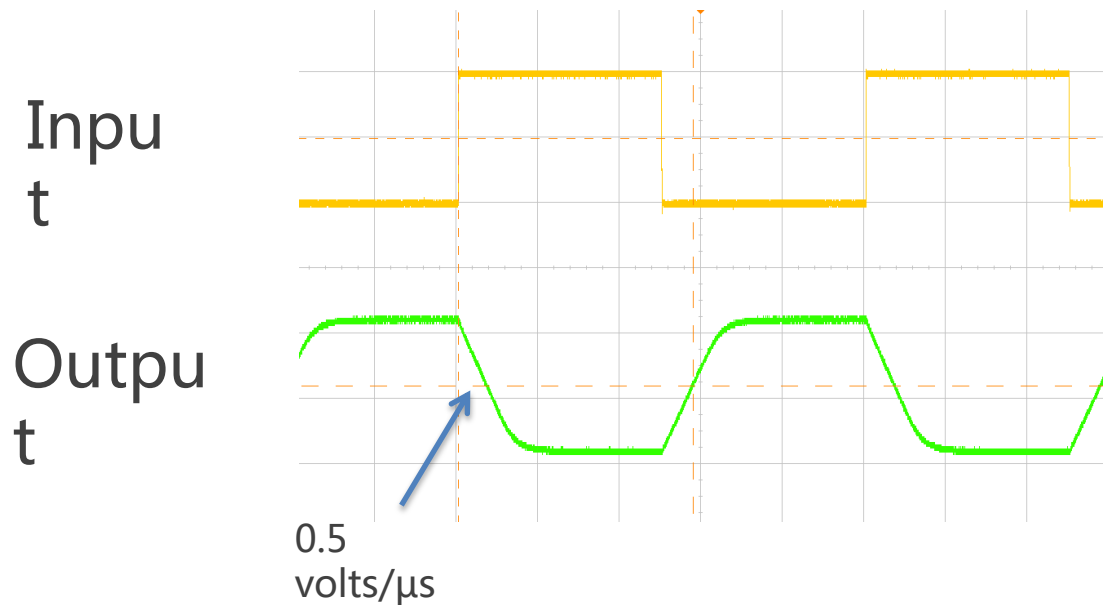The LM741 has a slew rate of 0.5 volts/ μ s



The maximum frequency input sine which can be applied before slew rate distortion is seen-


$$\frac{dV}{dt}(\sin(2\pi ft)) = 2\pi f \cos(2\pi ft)$$

$$\frac{dV}{dt}(max) = 2\pi f$$

$$f_{max} = \frac{10^6 * Slew Rate}{2\pi}$$

Input

Output

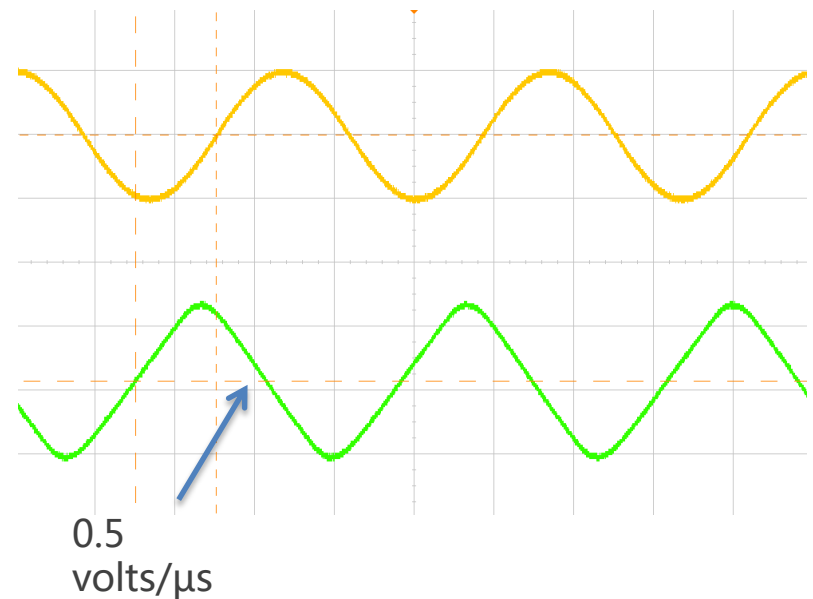




Purchasing an Op-amp

- Package
 - DIP
 - TSSOP
 - MSOP
- Mount Type
 - Surface Mount
 - Through Hole



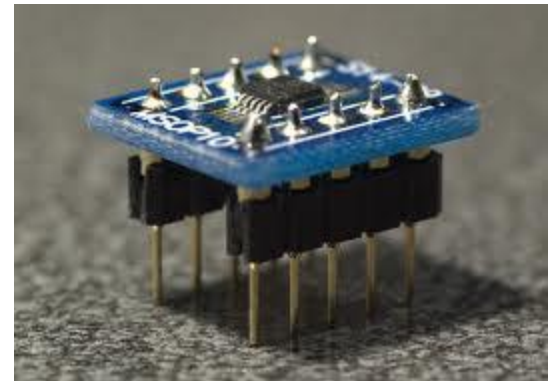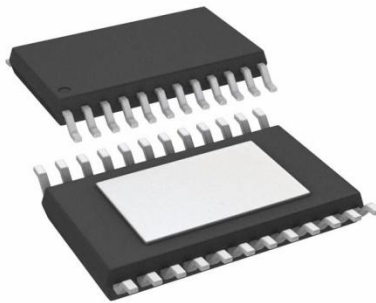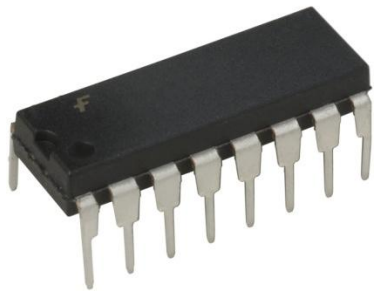1. Package

- Dual in-line-package (DIP):
Regular sized op amp.
- Thin Shrink Small outline package (TSSOP):
Smaller body size & lead pitches (0.9mm thick).
- Micro small outline package (MSOP):
Only 3mm * 5mm



2. Mount type

- Surface mount

SOPs are surface mount.
Need sockets to solder
on the PCB.

- Through hole

DIPs are through hole.
Sockets will help to
remove or switch the
op amp.



Conclusion

Cheng - History

Pat - OP AMP Construction/design

Alex - OP Amp Application Circuits

Ken - Effect of Input offset voltage

Nan - Effect of Slew Rate, Packaging, Conclusion



Thank you

